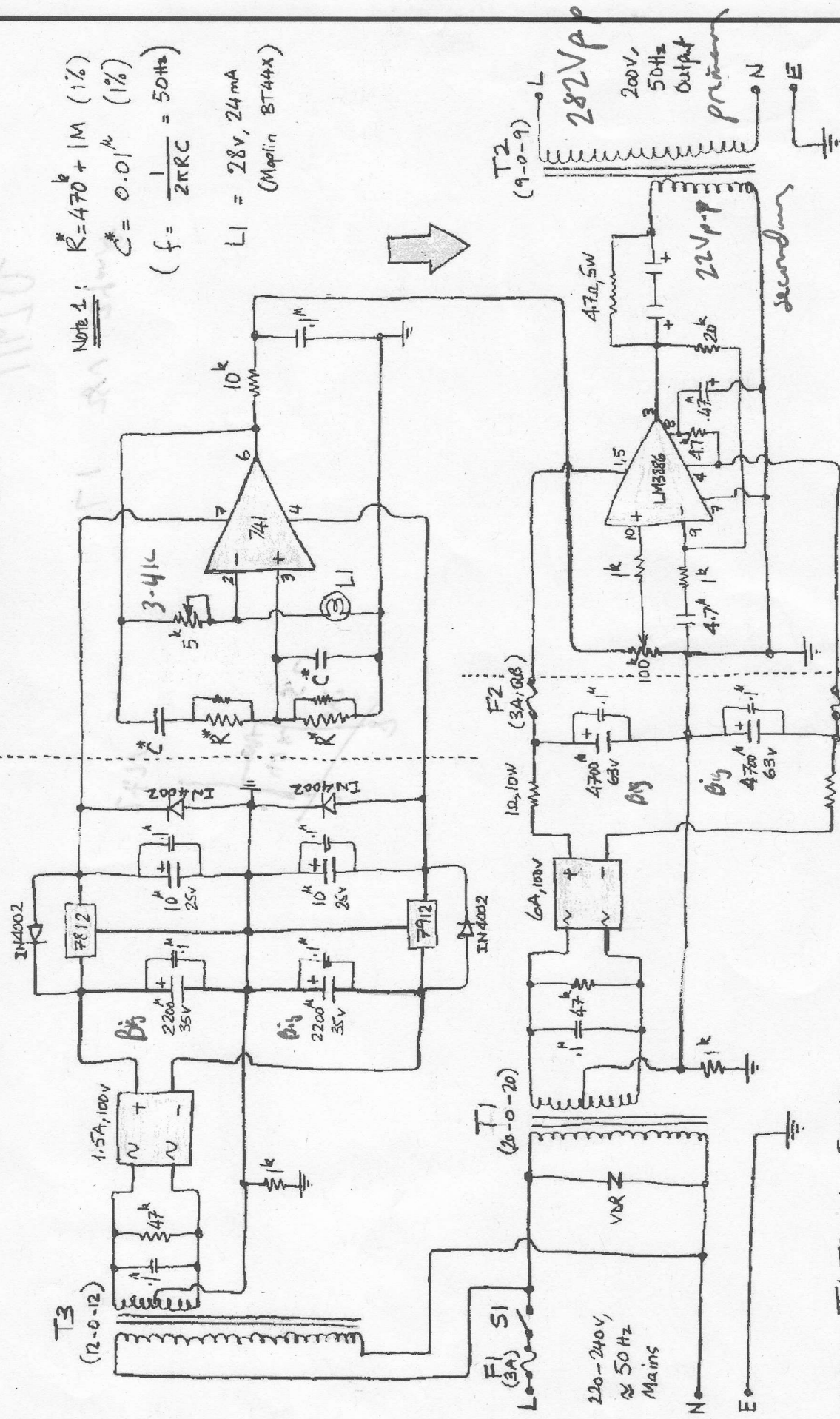


Precision DIY Power supply for Garrard 401 Turntable

OS POWER SUPPLY ← → OSCILLATOR (OS)



PA POWER SUPPLY ← → POWER AMP (PA)

Designed by Dr M. S. Imbabi, and posted 5th December 2000